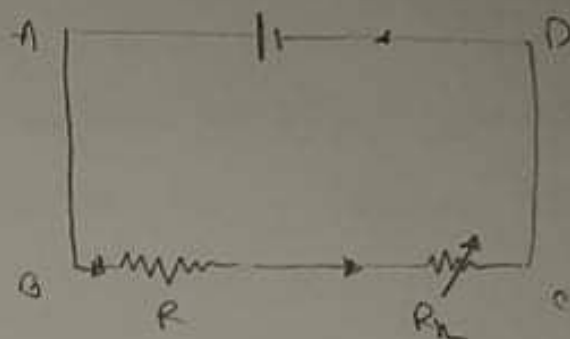


Ans. to the Qno-'a'

Here, given is,

fixed resistance, $R = 10\Omega$

variable " , $R_h = 2\Omega$



Now,

$$\text{Current flow of the circuit, } I = \frac{V}{R + R_h}$$
$$= \left(\frac{12}{10 + 2} \right) \text{ A}$$

$$\therefore I = 1 \text{ A.}$$

\therefore Flow of current in the circuit of fig-1 is 1 A.

Ans. to the Qno-'b'

Given, variable resistance, $R_h = 2\Omega$

fixed " , $R = 10\Omega$.

Voltage, $V = 12\text{V}$

Flow of current, $I = 1 \text{ A}$ [From 'a']

Now,

$$\text{Potential drop across } R, V_R = I \cdot R$$
$$= (1 \times 10) \text{ V}$$

$$\therefore V_R = 10 \text{ V.}$$

\therefore Potential drop across R is 10 volts.

Ans. to the Q no. 'c'


Let, potential drop across R is V_R .

For different values of R_h (from 2 to 20), graph of potential drop across R vs variable resistance R_h is drawn as follows:

We know, Potential drop across R ,

$$V_R = \frac{R}{R + R_h} \times V$$

| | | | | | | | | | | |
|----------------|----|------|-----|------|----|------|----|------|------|----|
| $R_h (\Omega)$ | 2 | 4 | 6 | 8 | 10 | 12 | 14 | 16 | 18 | 20 |
| $V_R (V)$ | 10 | 8.57 | 7.5 | 6.67 | 6 | 5.45 | 5 | 4.61 | 4.28 | 4 |

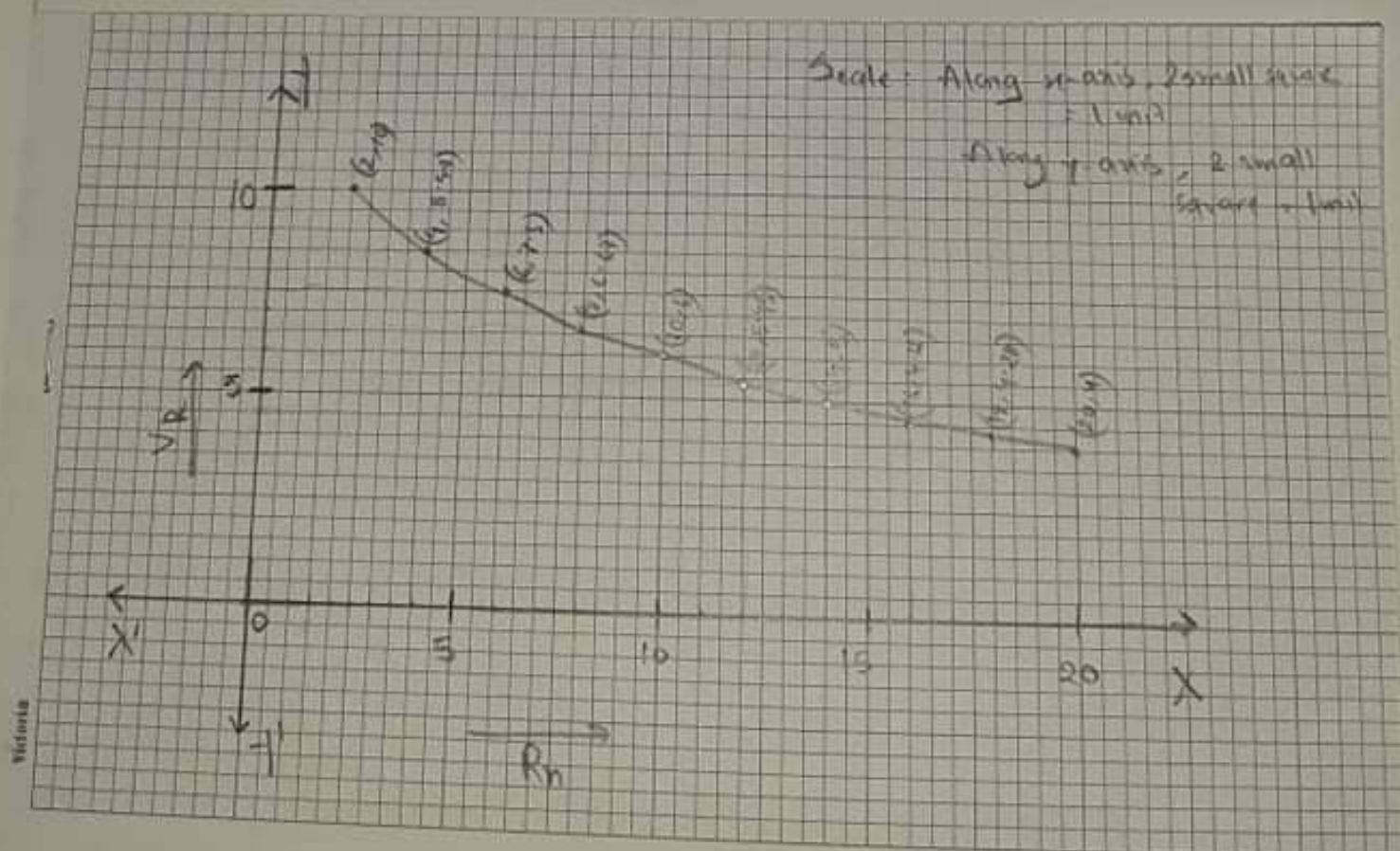

Here, XOX' and YOY' represent x -axis and y -axis respectively. Along x -axis and y -axis, 2 small squares = 1 unit. We plot the values of R_h along x -axis and values of V_R along y -axis. Thus required graph is drawn.

In the graph we can see that when the variable resistance R_h is equal to 2Ω , then potential drop across R is maximum.

\therefore Maximum potential drop across $R = 10V$.

Ans. to the Qno-'d'

Given, Voltage, $V = 12V$

Fixed Resistance, $R = 10\Omega$

Variable resistance, $R_h = 2\Omega$

Time, $t = 1s$.


\therefore Current flow, $I = \frac{V}{R + R_h}$.

Again, Heat produced, $W = I^2 R t$

\therefore Heat produced across R_h is, $W_h = I^2 R_h t$.

Now, for different values of R_h we will find out the values of I then the values of W_h and plot them. The table for the values:

| | | | | | | |
|----------------|---|-------|-----|-----|-------|-----|
| $R_h (\Omega)$ | 2 | 6 | 10 | 14 | 18 | 20 |
| $I (A)$ | 1 | 0.75 | 0.6 | 0.5 | 0.429 | 0.4 |
| $W_h (J)$ | 2 | 3.375 | 3.6 | 3.5 | 3.313 | 3.2 |

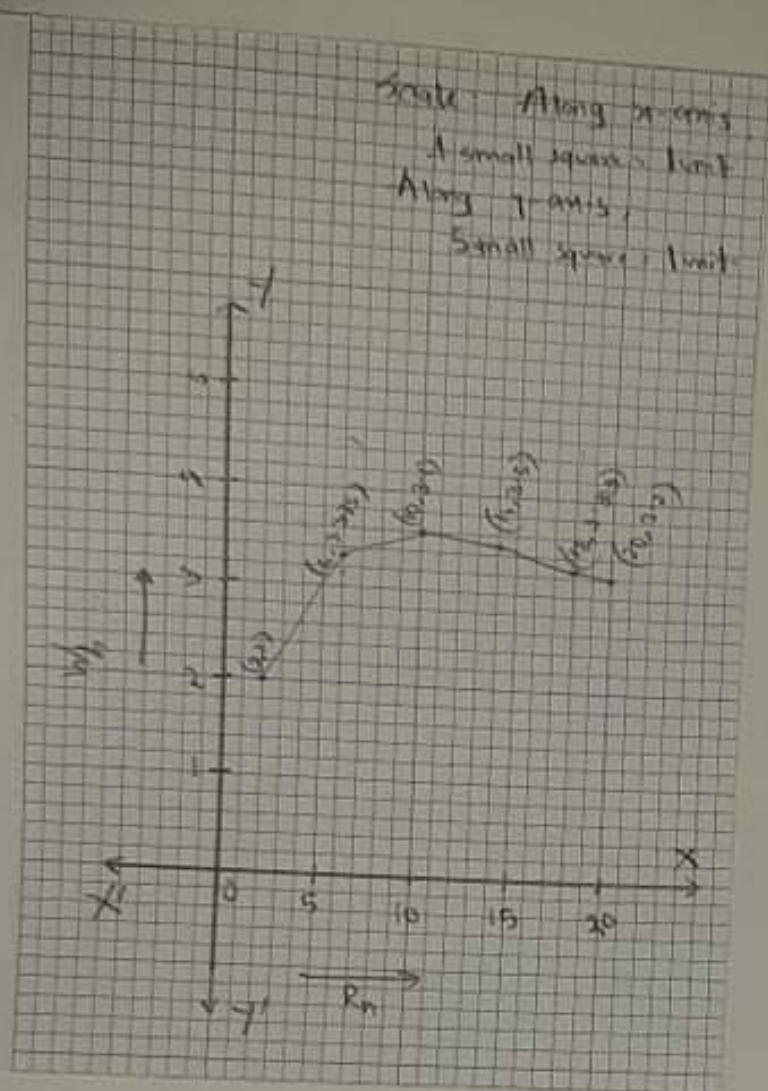

Here, XOX' and YOY' represent x-axis and y-axis respectively. O is the origin. Along x-axis, 1 small square = 1 unit and along y-axis, 5 small square = 1 unit. We plot the values of R_h along x-axis and values of W_h along y-axis.

Thus our required graph is drawn.

In the graph, we can see that, when the value of R_h is 10-2, maximum heat^{is} produced then which is 3.6 J.

\therefore Maximum heat produced across R_h @ per second = 3.6 J.

Ans. to the Qn'a'e'

According to the condition, the circuit of fig-2 is connected with AB part of fig-1.

Here, let,

$$R_1 = 6\Omega$$

$$R_2 = 4\Omega$$

$$R_3 = \cancel{10\Omega} 3\Omega$$

$$R_4 = \cancel{7\Omega} \text{ and } R = 10\Omega, R_h = 2\Omega.$$

Now, as R_1 and R_2 are connected in series,

$$\begin{aligned} \therefore R_{s1} &= R_1 + R_2 \\ &= (6 + 4)\Omega \end{aligned}$$

$$\therefore R_{s1} = 10\Omega.$$

Again, R_3 and R_4 are connected in series,


$$\begin{aligned} \therefore R_{s2} &= R_3 + R_4 \\ &= (3 + 7)\Omega \end{aligned}$$

$$\therefore R_{s2} = 10\Omega.$$


Now, R_{s1} and R_{s2} are in parallel connection.

$$\begin{aligned} \therefore \frac{1}{R_p} &= \frac{1}{R_{s1}} + \frac{1}{R_{s2}} \\ &= \frac{1}{10} + \frac{1}{10} = \frac{2}{10} \frac{1}{5} \end{aligned}$$

$$\therefore R_p = 5\Omega.$$

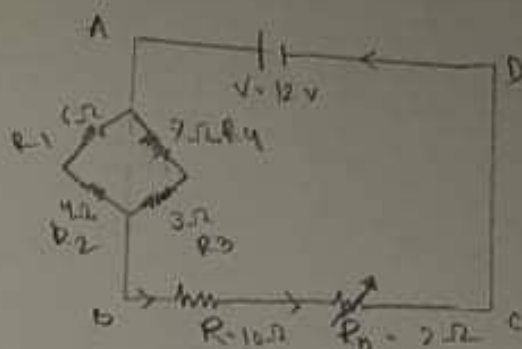

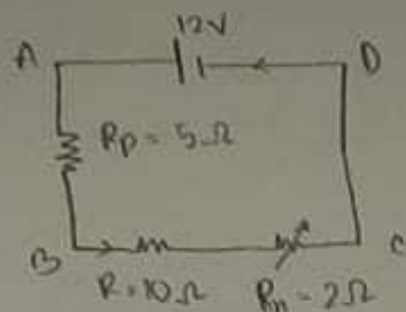If we draw the circuit again with R_p as equivalent resistance,



Now, Potential drop across R , $V_R' = \frac{R}{R_p + R + R_n} \times V$

$$= \left(\frac{10}{5 + 10 + 2} \times 12 \right) V$$

$$= 7.06 V$$

∴ Potential drop across R , $V_R' = 7.06 V$.

From 'b' we got that, potential difference across R is 10V.


So, we can see that potential difference across R has decreased when circuit of fig. 2 has been added.

So, potential difference will change and the amount of change of potential drop across $R = (10 - 7.06) V$

$$= 2.94 V$$

Ans. to the Qno-1)

From 'b' we get,

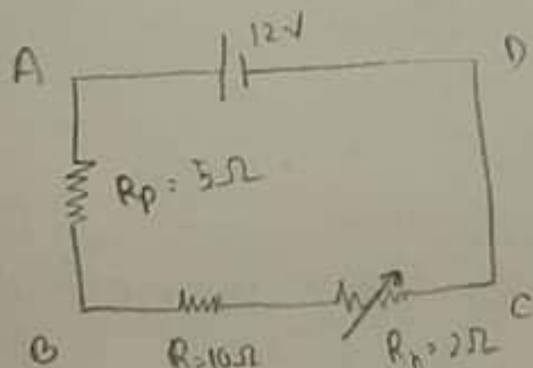

Equivalent resistance of the circuit drawn,

$$\begin{aligned} R_E &= R_p + R + R_h \\ &= (5 + 10 + 2) \Omega \\ &= 17 \Omega \end{aligned}$$

We know, current flow, $I = \frac{V}{R_E}$

$$= \frac{12}{17} = 0.706 \text{ A.}$$

Produced heat, $W = I^2 R t$

$$= (0.706^2 \times 17 \times 5) \text{ J}$$

$\therefore W = 42.36 \text{ J.}$

[Here, $t = 5 \text{ s}$
 $I = 0.706 \text{ A}$
 $R_E = 17 \Omega$]

Now, mass of water, $m = 5 \text{ kg}$.

Specific heat capacity, $s = 4200 \text{ J kg}^{-1} \text{ K}^{-1}$.

Amount of heat produced, $W = H = 42.36 \text{ J}$.

We know,

Heat absorbed by water, $H = ms \Delta \theta$ [where θ is temperature]

$$\therefore, 42.36 = 5 \times 4200 \times \Delta \theta$$

$$\therefore, \Delta \theta = \frac{42.36}{5 \times 4200}$$

$$= 2.01 \times 10^{-3} \text{ K.}$$

Again to increase the same amount of temperature in half the time, amount of resistance needed is R .

$$\text{Time, } t' = \frac{t}{2} = \frac{5}{2} = 2.5 \text{ s.}$$

Now,

$$I^2 R' t' = 42.36$$

$$\text{or, } R' = \frac{42.36}{0.706^2 \times 2.5}$$

$$= 33.99 \, \Omega$$

$$\therefore R' \approx 34 \, \Omega.$$

\therefore To increase the same amount of temp. of water in half the time, i.e., in 2.5 s the resistance has to be $34 \, \Omega$.

$$\begin{aligned} \therefore \text{Change in resistance} &= (34 - 17) \, \Omega \\ &= 17 \, \Omega. \end{aligned}$$